

Circuit Theory and Electronics Fundamentals

Department of Electrical and Computer Engineering, Técnico, University of Lisbon

Laboratory Report

João Delile nº95800

José Murteira nº96547

Manuel Candeias nº97259

May 24, 2021

Contents

1 Introduction

In this laboratory assignment the objective is to study an amplifier together with some of its properties, namely the input and output impedances, the voltage gain and also the influence of the frequency on this gain. The specific circuit used in the Octave and Ngspice software is the one illustrated:

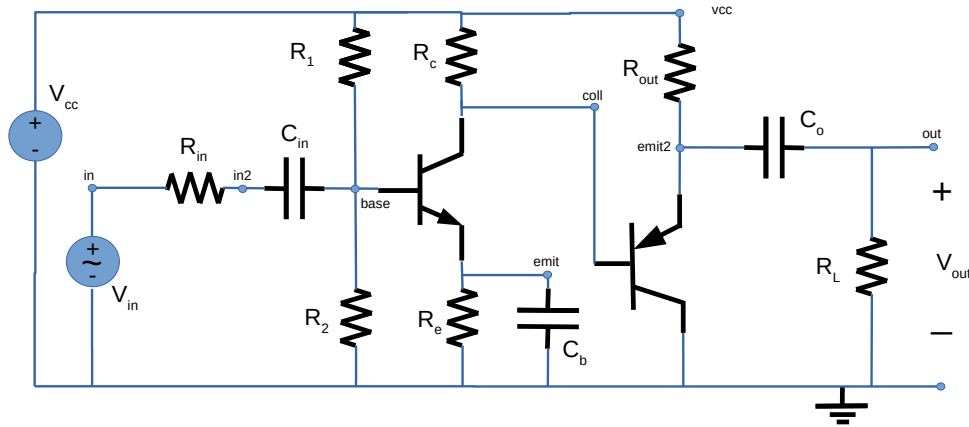


Figure 1: Amplifier circuit

The use of an amplifier generally means the ability to obtain an output signal with a greater amplitude in relation to its source signal. An example of using this type of circuit is the simplest microphones that can be found on the market.

2 Theoretical Analysis

In this section we will detail the theoretical study of the Amplifier Circuit conducted during this lab. The circuit was divided into two separate ones: the gain stage and the output stage. The first one increased the gain, but it had a drop of current considered undesirable due to the output impedance. The latter one corrects this effect while having a gain near one, as to not decrease the voltage previously gained.

The entire circuit can be seen in the following image:

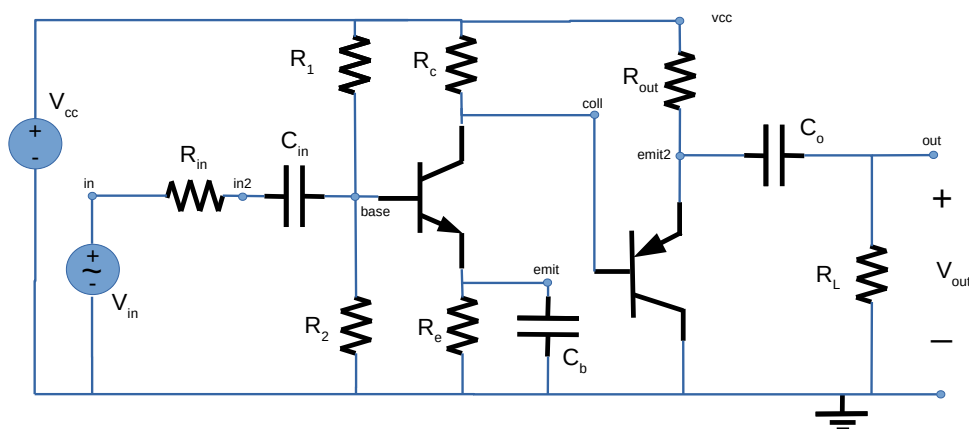


Figure 2: Amplifier circuit

One must note that V_{in} and R_{in} constitute the thevenin equivalent of the circuit to which the amplifier is connected.

The capacitor connected to R_{in} will enforce that only the AC part of the voltage is taken into account. The DC part is supplied by a constant 12V voltage source V_{cc} . With this architecture, we can ensure that the transistors are in forward active region (FAC), for the V_{cc} will force an voltage drop bigger than the one necessary for that mode of operation.

It was used an Operating Point analysis where the DC component of the current and voltage is taken into account, but not the AC one, followed by an Incremental Analysis where the AC component of the current and voltage is taken and where a linear model of the transistor is assumed. By adding the results, we can obtain a solution for the circuit, thereby obtaining the values necessary to compute the theoretical gain of the amplifier and the various impedances, such as the input and output ones. The analysis can be divided into the following particular smaller analysis:

- Operating Point analysis for the gain stage;
- Incremental analysis for the gain stage;
- Calculation of the gain for the gain stage;
- Operating Point analysis for the output stage;
- Incremental analysis for the output stage;
- Calculation of the gain for the output stage;
- Calculation of the input and output impedances;

To calculate the OP of each stage, it was considered the following circuits for each stage:
[Insert images of OP analysis]

It was used the mesh method in conjunction with the Ebers-Moll bipolar npn transistor model in order to calculate the currents in each mesh and the voltage drops between nodes. With this, it was possible to calculate the DC component of the output voltage.

To calculate the incremental stage, it was considered the following incremental model of the transistor:

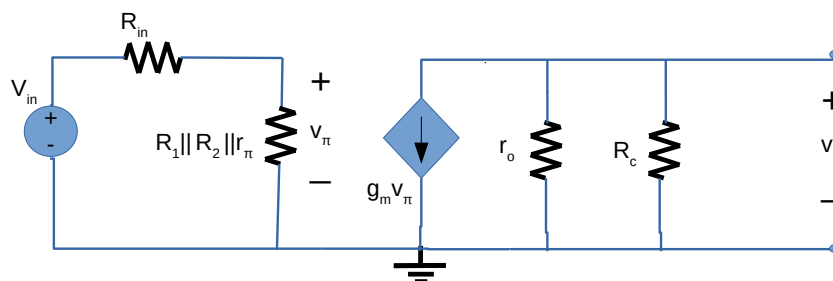


Figure 3: Amplifier circuit

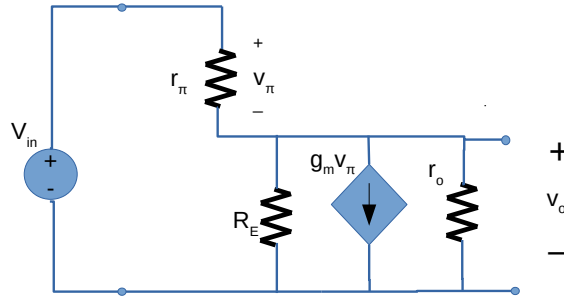


Figure 4: Amplifier circuit

Each stage was therefore modeled as follows:

$$g_m = I_C/V_T \quad (1)$$

$$r_{pi} = \beta_F/g_m \quad (2)$$

$$r_o = V_A/I_C \quad (3)$$

By using the mesh method, it was possible to calculate the AC component for the output voltage.

The total voltage for each frequency is equal to the sum of the AC with the DC component.

This analysis was repeated for various frequencies of V_{in} (10 equally spaced frequencies per decade), and the results were plotted on a dB scale. The calculation of the overall gain was obtained by multiplying the gain of each stage. The results can be observed in the following graphs:

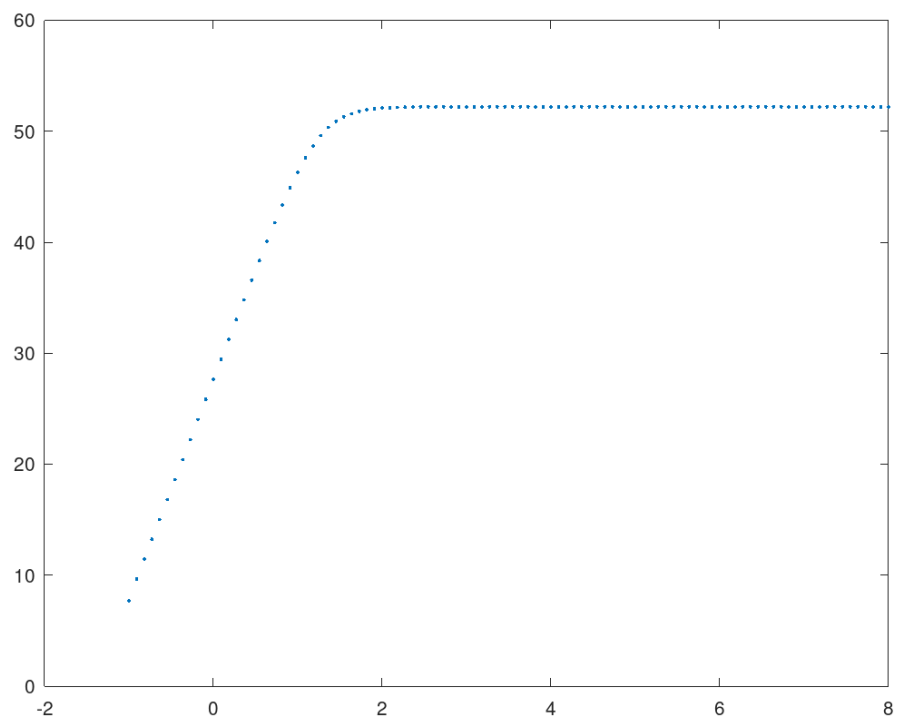


Figure 5: Amplifier circuit

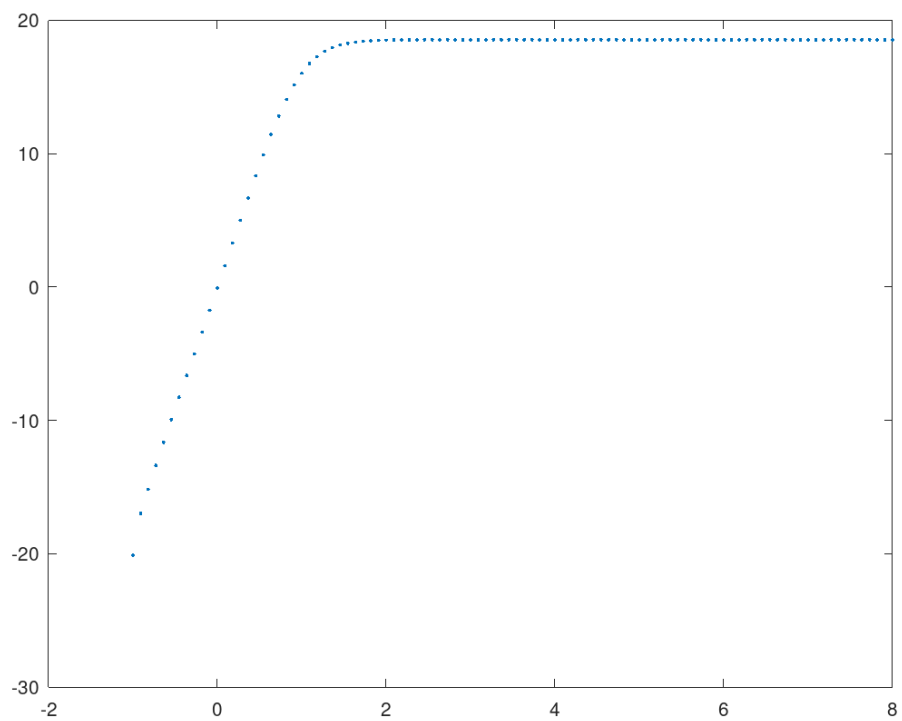


Figure 6: Amplifier circuit

3 Simulation Analysis

In the simulation study of an amplifier circuit, the Ngspice software was used, where some modifications were made to the script initially made available in order to obtain the best merit in this work. For this and also as a requirement, the NPN and PNP models were used for the transistors, referring to the Gain stage and the Output stage, respectively.

From operating point analysis we got the following results:

low	2.513670e+00
cost	7.109638e+03
gain	1.487926e+01
bandwidth	3.136186e+06
merit	2.611124e+03

Table 1: Voltages

And now for the impedances values, the input and output impedances, respectively:

zin
2.738309e+00

Table 2: Voltages

4 Comparisons

In this section, a comparison between the ngspice and octave results is made. Moreover, we delve into the reasons regarding the differences and similarities observed

And now for the impedances values, in the tables down below we can compare side by side:

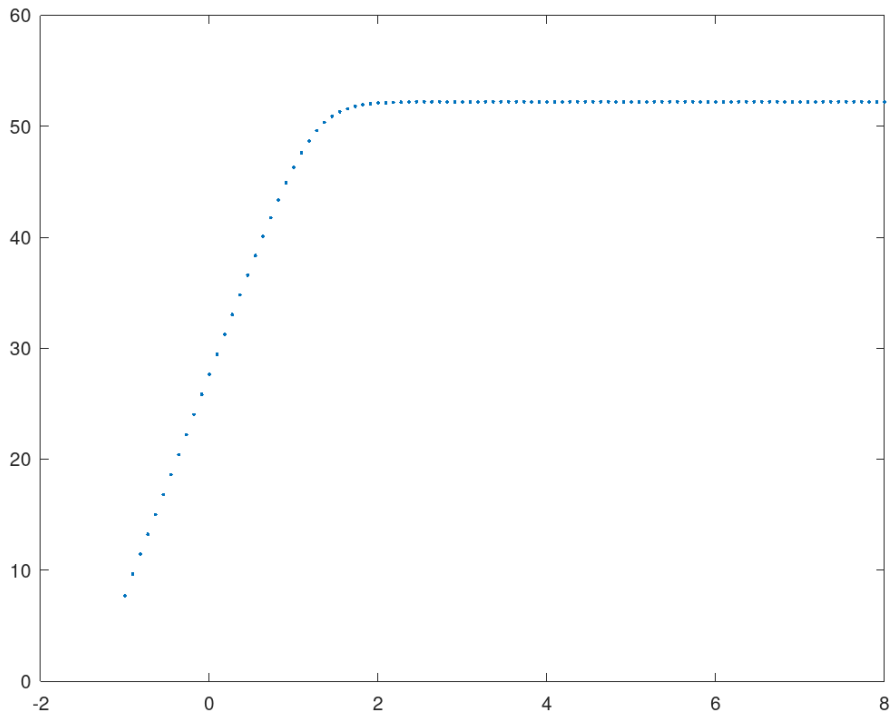


Figure 7: Amplifier circuit

zin
2.738309e+00

Table 3: Input Impedance by Ngspice

Z_{in}	Z_{out}
115705 Ω	3.25315 Ω

Table 4: Input and Output Impedances by Octave

Comparing both results, we can see that the gain is not the same. Such a disparity is visibly noticeable for high frequencies, where the gain drops in the simulation, but stabilizes in the theoretical analysis. Such a result can be explained when one notices that gain was obtained by assuming a linear incremental model. This model is based on truncating the Taylor series for each component, so that the circuit components can all have a linear dependency on frequency. However, such is an approximation and, in this case, the error grows with the frequency, for transistors are non-linear devices that depend on it. By analysing the incremental model, one notes that only the capacitors present have a dependency on frequency, the transistor does not. Since the impedance of the capacitors will decrease with the rise in frequency, it eventually becomes negligible and the gain stabilizes.

It is also possible to see that the maximum gain is not the same, growing much quicker in the ngspice model, stabilizing at a lower frequency and at a higher value.

The impedances are

5 Conclusion

We then concluded our laboratory work, corresponding to all the criteria initially proposed. It is true that there are discrepancies between the two different set of results, but these are discussed in the section of comparisons.

References

- [1] K. Mayaram (1988) in 'DC and transient analyses' *CODECS: A Mixed-Level Circuit and Device Simulator*, Memorandum No. UCB/ERL M88/71 Berkeley , p.23
<http://www.eecs.berkeley.edu/Pubs/TechRpts/1988/ERL-88-71.pdf>